TSEK06 High-Level Design Report

Group 5

Editor: Johannes Klasson

Version P1B

Status

Reviewed	Johannes Klasson	2016-02-15
Approved	Martin Nielsen-Lönn	-

PROJECT IDENTITY

 $\begin{tabular}{ll} VT, 2016, Group 5 \\ Linköpings Tekniska Högskola, ISY \end{tabular}$

${\bf Group\ members}$

Name	Responsibility	Phone	E-mail
Johan Isaksson	Project Leader	070-2688785	johis024@student.liu.se
Johannes Klasson	Document Manager	073-8209003	johkl226@student.liu.se
Jonas Tarasso	Designer	070-5738583	jonta760@student.liu.se
Alexander Yngve	Designer	076-2749762	aleyn573@student.liu.se

 $\mathbf{Customer} \colon \mathrm{ISY}$

Contact at customer: Martin Nielsen-Lönn Course resposible: Atila Alvandpour Consultant: Martin Nielsen-Lönn

Contents

1	Intr	roduction	1
2		ck Level Description	1
	2.1	SPI/PSRBR	1
	2.2	16-bit Kogge-Stone Adder	1
		2.2.1 Red	1
		2.2.2 Yellow	3
		2.2.3 Yellow with carry	4
		2.2.4 Sum	4
	2.3	Comparator	5
3	Sim	ulation Results	6
	3.1	SPI In	6
		3.1.1 Recieve	6
		3.1.2 Hanken 2	6
		3.1.3 Hanken 3	6
	3.2	Kogge-Stone Adder	6
	3.3	SPI Out	6
	3.4	Comparator	6
	3.5	Top Level	6
	5.5	Top Level	U
4	Risl	ks and Delays	6
\mathbf{A}	Tim	ne Report	6

CONTENTS February 16, 2016

Document history

Version	Date	Changes	Performed by
P1A	2016-02-15	First draft	Johan Isaksson

1 Introduction

2 Block Level Description

2.1 SPI/PSRBR

2.2 16-bit Kogge-Stone Adder

The Kogge-Stone adder consists of four simple blocks connected in a complex way.

Lägg till bild på hur blocken sitter ihop och förklaring om P och G signalerna.

2.2.1 Red

Table 1 – Logic table of red block.

A_i	B_i	$P = A_i \oplus B_i$	$G = A_i \wedge B_i$
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

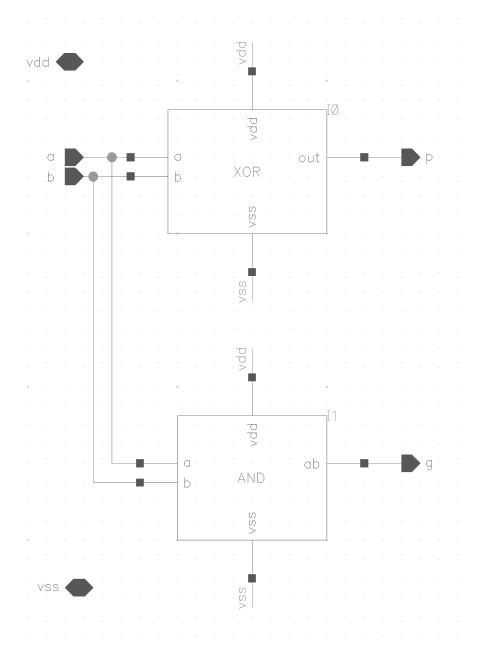


Figure 1 – Schematic view of the red block.

2.2.2 Yellow

G_i	$G_{i,prev}$	P_i	$P_{i,prev}$	$P = P_i \wedge P_{i,prev}$	$G = (P_i \land G_{i,prev}) \lor G_i$
0	0	0	0	0	0
0	0	0	1	0	0
0	0	1	0	0	0
0	0	1	1	1	0
0	1	0	0	0	0
0	1	0	1	0	0
0	1	1	0	0	1
0	1	1	1	1	1
1	0	0	0	0	1
1	0	0	1	0	1
1	0	1	0	0	1
1	0	1	1	1	1
1	1	0	0	0	1
1	1	0	1	0	1
1	1	1	0	0	1
_1	1	1	1	1	1


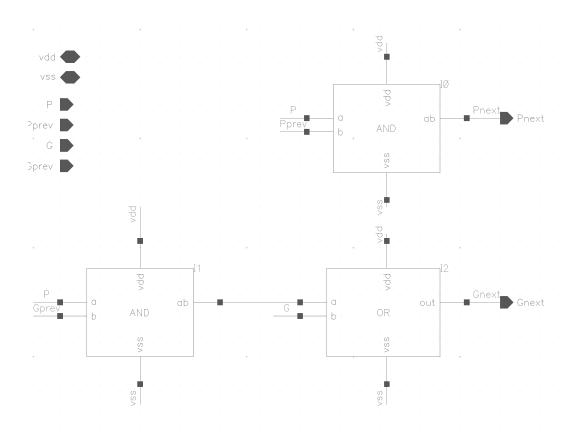


Figure 2 – Schematic view of the yellow block.

2.2.3 Yellow with carry

Table 3 – Logic table of yellow with carry block.

P_i	G_i	$G_{i,prev}$	$G = (P_i \wedge G_{i,prev}) \vee G_i$
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

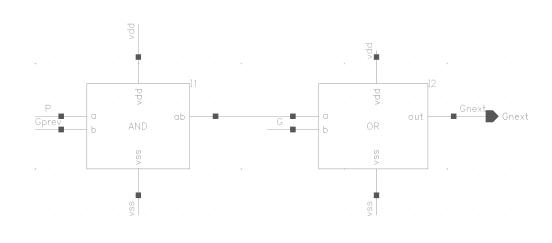


 ${\bf Figure~3}-{\bf Schematic~view~of~the~yellow~carry~block}.$

2.2.4 Sum

 ${\bf Table}~{\bf 4}-{\rm Logic~table~of~sum~block}.$

P_i	C_{i-1}	$S_i = P_i \oplus C_{i-1}$
0	0	0
0	1	1
1	0	1
1	1	0

2.3 Comparator February 16, 2016

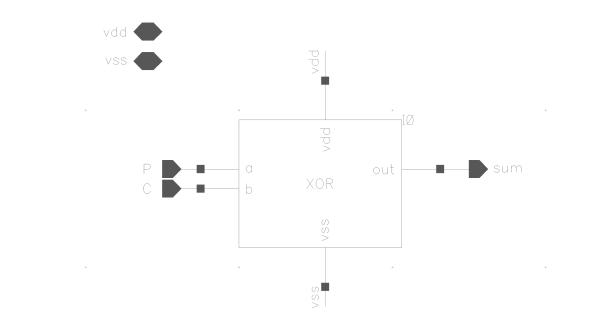

 ${\bf Figure}~{\bf 4}-{\rm Schematic~view~of~the~sum~block}.$

2.3 Comparator

Table 5 – Logic table of XNOR block.

A_i	B_i	$Y = \overline{(A_i \oplus B_i)}$
0	0	1
0	1	0
1	0	0
1	1	1

5

3 Simulation Results

- 3.1 SPI In
- 3.1.1 Recieve
- 3.1.2 Hanken 2
- 3.1.3 Hanken 3
- 3.2 Kogge-Stone Adder
- 3.3 SPI Out
- 3.4 Comparator
- 3.5 Top Level
- 4 Risks and Delays
- A Time Report