

TSEK06 High-Level Design Report

Group 5

Editor: Johannes Klasson

Version P1B

Status

Reviewed	Johannes Klasson	2016-02-15
Approved	Martin Nielsen-Lönn	-

PROJECT IDENTITY

VT, 2016, Group 5
Linköpings Tekniska Högskola, ISY

Group members

Name	Responsibility	Phone	E-mail
Johan Isaksson	Project Leader	070-2688785	johis024@student.liu.se
Johannes Klasson	Document Manager	073-8209003	johkl226@student.liu.se
Jonas Tarasso	Designer	070-5738583	jonta760@student.liu.se
Alexander Yngve	Designer	076-2749762	aleyn573@student.liu.se

Customer: ISY
Contact at customer: Martin Nielsen-Lönn
Course responsible: Atila Alvandpour
Consultant: Martin Nielsen-Lönn

Contents

1	Introduction	1
2	Block Level Description	1
2.1	SPI/PSRBR	1
2.2	16-bit Kogge-Stone Adder	1
2.3	Comparator	5
3	Simulation Results	6
3.1	SPI In	6
3.1.1	Recieve	6
3.1.2	Hanken 2	6
3.1.3	Hanken 3	6
3.2	Kogge-Stone Adder	6
3.3	SPI Out	6
3.4	Comparator	6
3.5	Top Level	6
4	Risks and Delays	6
A	Time Plan	6
B	Time Report	6

Document history

Version	Date	Changes	Performed by
P1A	2016-02-15	First draft	Johan Isaksson

1 Introduction

2 Block Level Description

2.1 SPI/PSRBR

2.2 16-bit Kogge-Stone Adder

The Kogge-Stone adder consists of four simple blocks connected in a complex way. These four blocks can be seen in figure 1-4. The red block constitute the initial stage which takes two binary numbers A and B as input. The corresponding truth table is found in table 1. The output signals P and G generated from this block are later used by other blocks in the adder. The G , also called the Generate signal, trickles down through the hierarchy of yellow, and yellow carry blocks to finally end up in the sum block. The truth table for this block can be found in table 4. Truth tables for the yellow and yellow carry blocks are found in table 2 and 3.

Lägg till bild på hur blocken sitter ihop.

Table 1 – Logic table of red block.

A_i	B_i	$P = A_i \oplus B_i$	$G = A_i \wedge B_i$
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

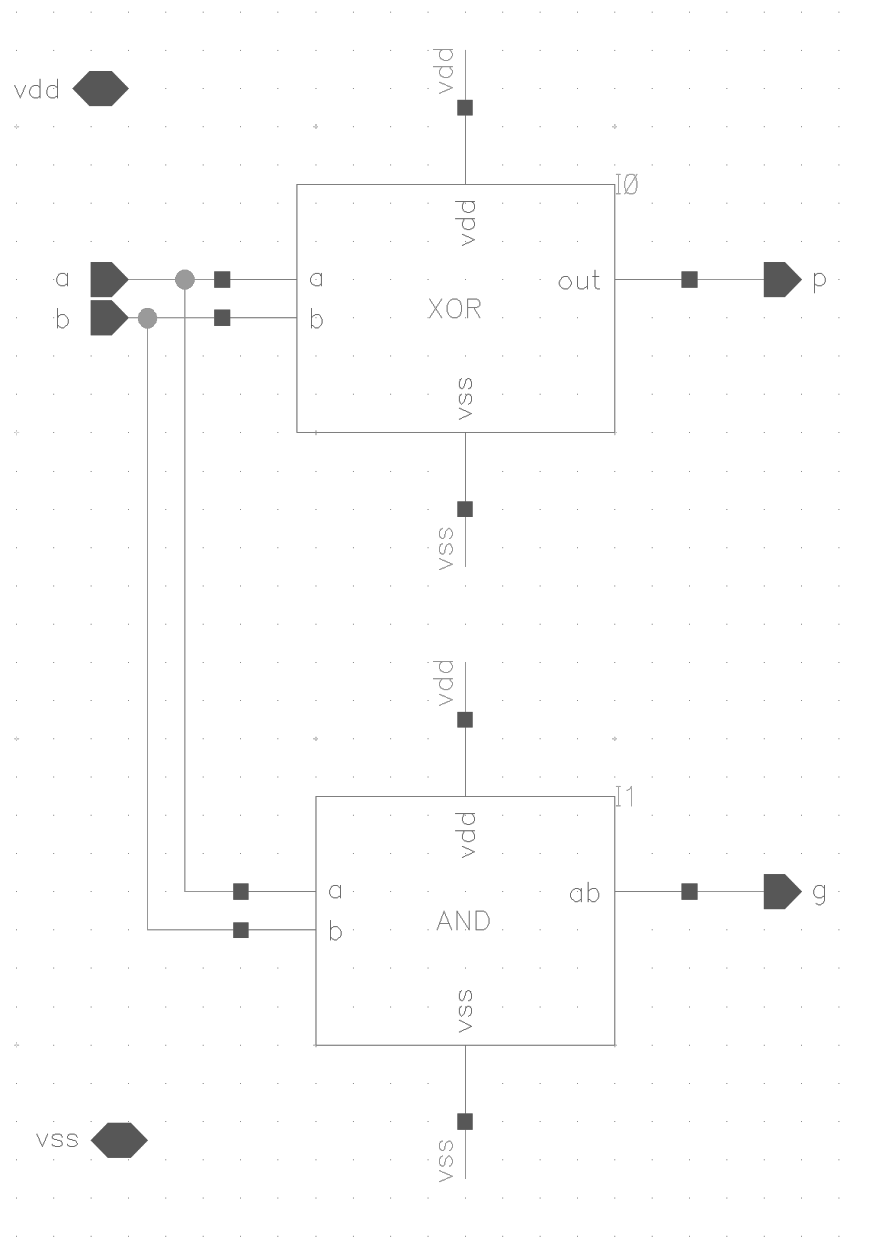


Figure 1 – Schematic view of the red block.

Table 2 – Logic table of yellow block.

G_i	$G_{i,prev}$	P_i	$P_{i,prev}$	$P = P_i \wedge P_{i,prev}$	$G = (P_i \wedge G_{i,prev}) \vee G_i$
0	0	0	0	0	0
0	0	0	1	0	0
0	0	1	0	0	0
0	0	1	1	1	0
0	1	0	0	0	0
0	1	0	1	0	0
0	1	1	0	0	1
0	1	1	1	1	1
1	0	0	0	0	1
1	0	0	1	0	1
1	0	1	0	0	1
1	0	1	1	1	1
1	1	0	0	0	1
1	1	0	1	0	1
1	1	1	0	0	1
1	1	1	1	1	1

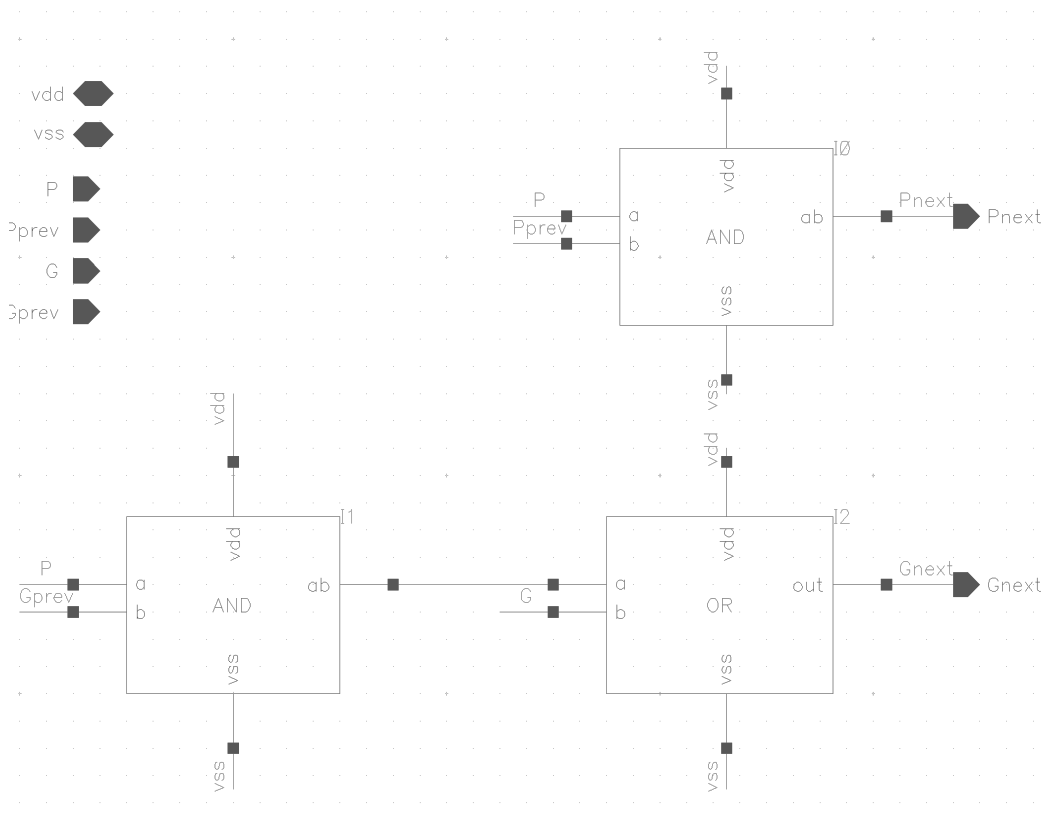
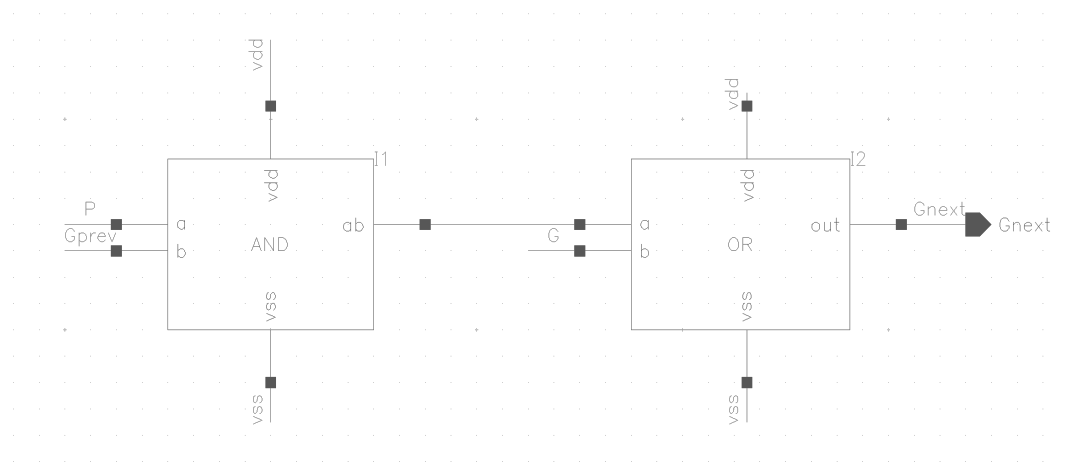
**Figure 2** – Schematic view of the yellow block.

Table 3 – Logic table of yellow with carry block.

P_i	G_i	$G_{i,prev}$	$G = (P_i \wedge G_{i,prev}) \vee G_i$
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

**Figure 3** – Schematic view of the yellow carry block.**Table 4** – Logic table of sum block.

P_i	C_{i-1}	$S_i = P_i \oplus C_{i-1}$
0	0	0
0	1	1
1	0	1
1	1	0

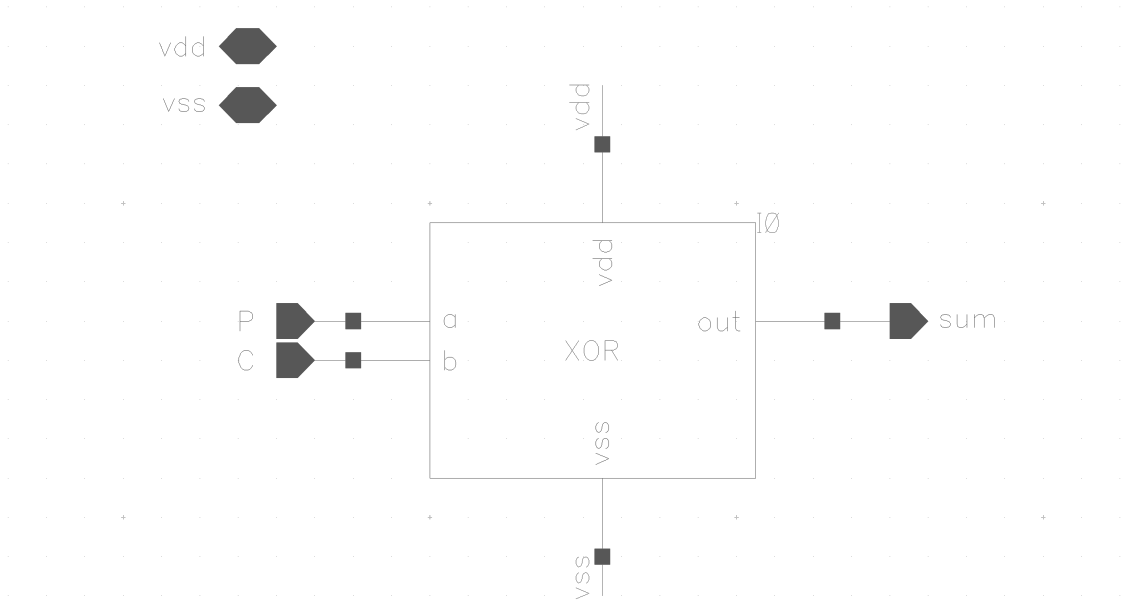


Figure 4 – Schematic view of the sum block.

2.3 Comparator

Table 5 – Logic table of XNOR block.

A_i	B_i	$Y = \overline{(A_i \oplus B_i)}$
0	0	1
0	1	0
1	0	0
1	1	1

3 Simulation Results

3.1 SPI In

3.1.1 Recieve

3.1.2 Hanken 2

3.1.3 Hanken 3

3.2 Kogge-Stone Adder

3.3 SPI Out

3.4 Comparator

3.5 Top Level

4 Risks and Delays

A Time Plan

B Time Report