

TSEK06 High-Level Design Report

Group 5

Editor: Johannes Klasson

Version P1B

Status

Reviewed	Johannes Klasson	2016-02-15
Approved	Martin Nielsen-Lönn	-

PROJECT IDENTITY

VT, 2016, Group 5
Linköpings Tekniska Högskola, ISY

Group members

Name	Responsibility	Phone	E-mail
Johan Isaksson	Project Leader	070-2688785	johis024@student.liu.se
Johannes Klasson	Document Manager	073-8209003	johkl226@student.liu.se
Jonas Tarasso	Designer	070-5738583	jonta760@student.liu.se
Alexander Yngve	Designer	076-2749762	aleyn573@student.liu.se

Customer: ISY
Contact at customer: Martin Nielsen-Lönn
Course responsible: Atila Alvandpour
Consultant: Martin Nielsen-Lönn

Contents

1	Introduction	1
2	Block Level Description	1
2.1	SPI/PSRBR	1
2.2	16-bit Kogge-Stone Adder	1
2.2.1	Red	1
2.3	Comparator	2
2.3.1	Yellow	2
2.3.2	Yellow with carry	3
2.3.3	Sum	3

Document history

Version	Date	Changes	Performed by
P1A	2016-02-15	First draft	Johan Isaksson

1 Introduction

2 Block Level Description

2.1 SPI/PSRBR

2.2 16-bit Kogge-Stone Adder

The Kogge-Stone adder consists of four simple blocks connected in a complex way.

Lägg till bild på hur blocken sitter ihop och förklaring om P och G signalerna.

2.2.1 Red

Table 1 – Logic table of red block.

A_i	B_i	$P = A_i \oplus B_i$	$G = A_i \wedge B_i$
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

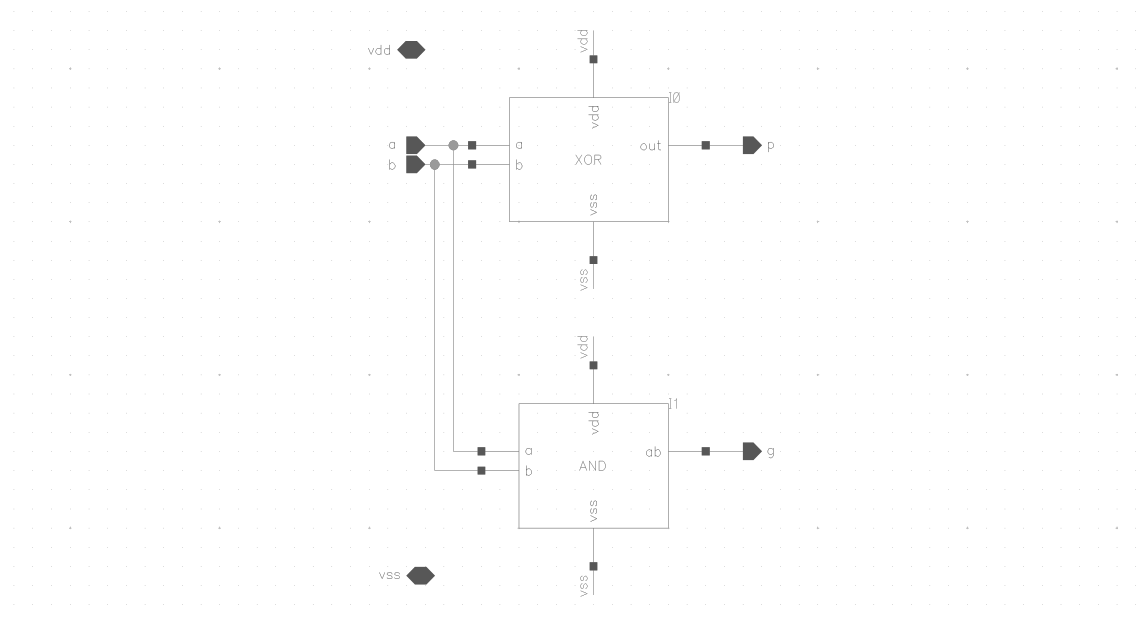


Figure 1 – Schematic view of the red block.

2.3 Comparator

2.3.1 Yellow

Table 2 – Logic table of yellow block.

G_i	$G_{i,prev}$	P_i	$P_{i,prev}$	$P = P_i \wedge P_{i,prev}$	$G = (P_i \wedge G_{i,prev}) \vee G_i$
0	0	0	0	0	0
0	0	0	1	0	0
0	0	1	0	0	0
0	0	1	1	1	0
0	1	0	0	0	0
0	1	0	1	0	0
0	1	1	0	0	1
0	1	1	1	1	1
1	0	0	0	0	1
1	0	0	1	0	1
1	0	1	0	0	1
1	0	1	1	1	1
1	1	0	0	0	1
1	1	0	1	0	1
1	1	1	0	0	1
1	1	1	1	1	1

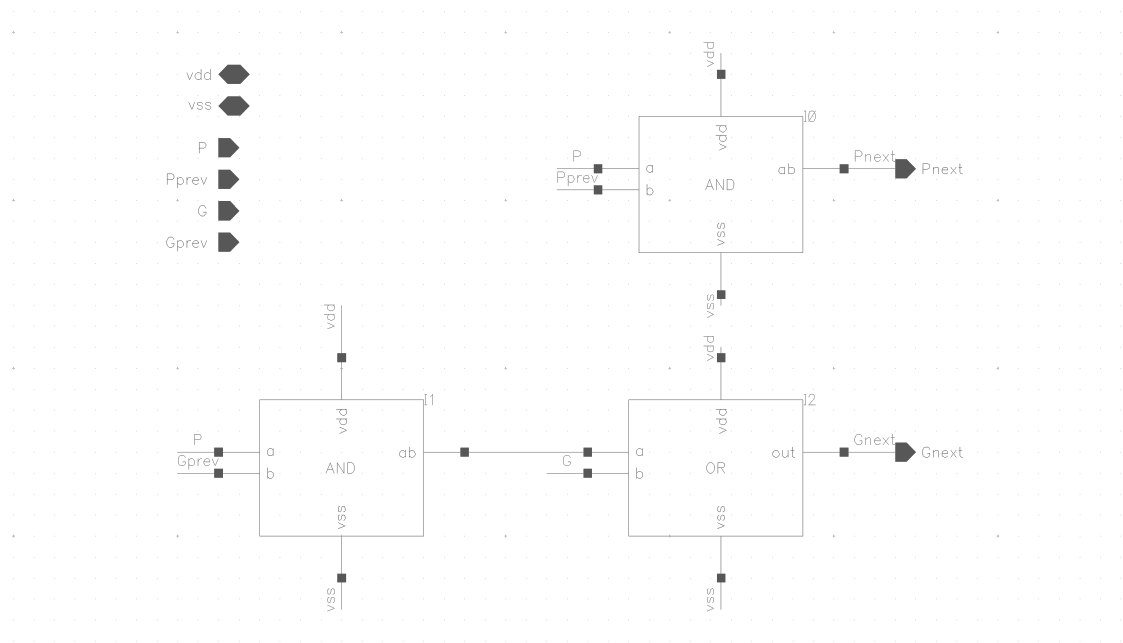


Figure 2 – Schematic view of the yellow block.

2.3.2 Yellow with carry

Table 3 – Logic table of yellow with carry block.

P_i	G_i	$G_{i,prev}$	Function2	Output
0	0	0	0	0
0	0	1	0	0
0	1	0	0	0
0	1	1	1	0
1	0	0	0	0
1	0	1	0	0
1	1	0	0	1
1	1	1	1	1

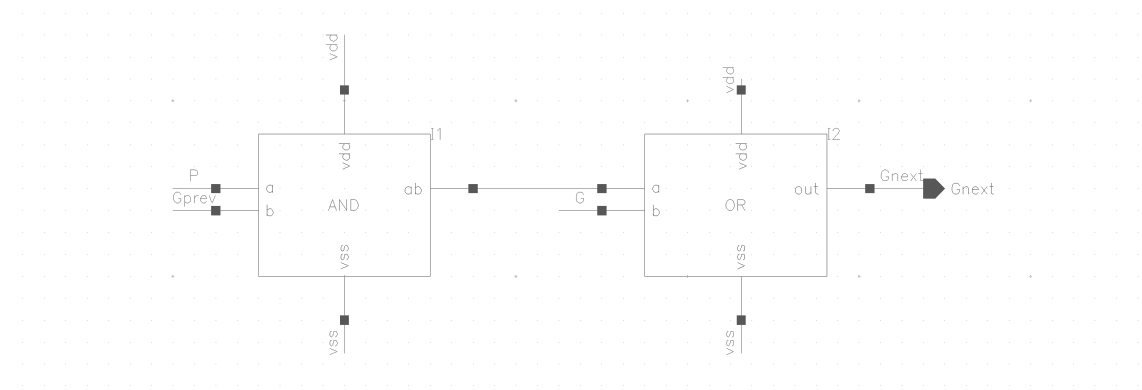


Figure 3 – Schematic view of the yellow carry block.

2.3.3 Sum

Table 4 – Logic table of sum block.

Input	Function1	Function2	Output
00	1	0	1
01	0	0	1
10	0	0	1
11	1	0	1

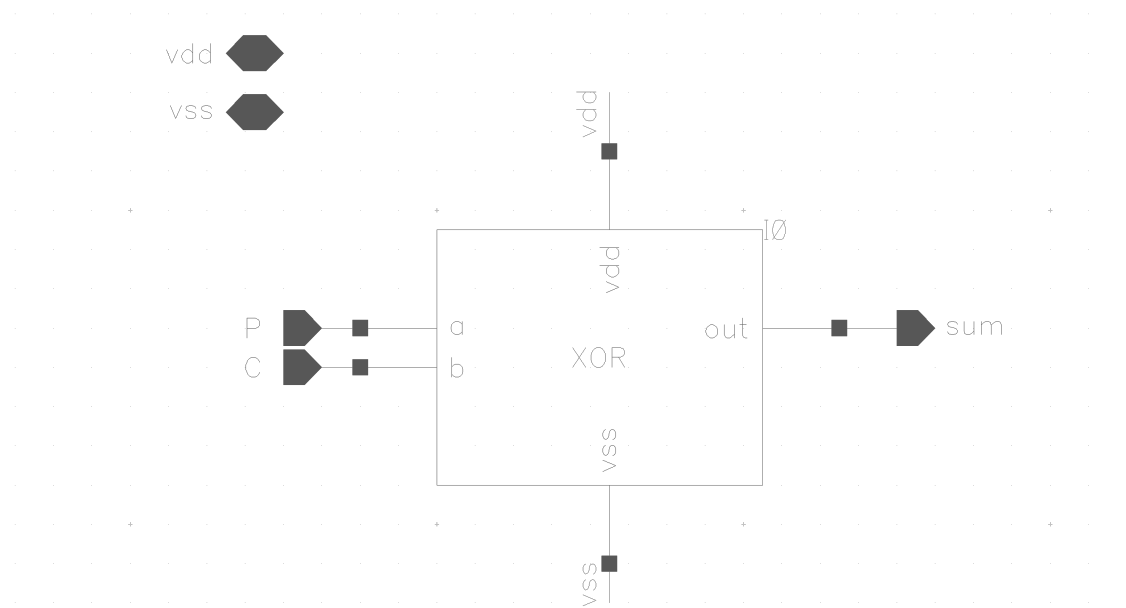


Figure 4 – Schematic view of the sum block.