TSEK06 High-Level Design Report

Group 5

Editor: Johannes Klasson

Version P1B

Status

Reviewed	Johannes Klasson	2016-02-15
Approved	Martin Nielsen-Lönn	-

PROJECT IDENTITY

 $\begin{tabular}{ll} VT, 2016, Group 5 \\ Linköpings Tekniska Högskola, ISY \end{tabular}$

${\bf Group\ members}$

Name	Responsibility	Phone	E-mail
Johan Isaksson	Project Leader	070-2688785	johis024@student.liu.se
Johannes Klasson	Document Manager	073-8209003	johkl226@student.liu.se
Jonas Tarasso	Designer	070-5738583	jonta760@student.liu.se
Alexander Yngve	Designer	076-2749762	aleyn573@student.liu.se

 $\mathbf{Customer} \colon \mathrm{ISY}$

Contact at customer: Martin Nielsen-Lönn Course resposible: Atila Alvandpour Consultant: Martin Nielsen-Lönn

Contents

1	Intr	roduction	1
2	Blo	ck Level Description	1
	2.1	SPI/PSRBR	1
		16-bit Kogge-Stone Adder	
		2.2.1 Red	1
	2.3	Comparator	3
		2.3.1 Yellow	
		2.3.2 Yellow with carry	3
		2.3.3 Sum	4

CONTENTS February 16, 2016

Document history

Version	Date	Changes	Performed by
P1A	2016-02-15	First draft	Johan Isaksson

1 Introduction

2 Block Level Description

2.1 SPI/PSRBR

2.2 16-bit Kogge-Stone Adder

The Kogge-Stone adder consists of four simple blocks connected in a complex way. Lägg till bild på hur blocken sitter ihop.

2.2.1 Red

Table 1 – Logic table of red block.

A_i	B_i	P	G
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

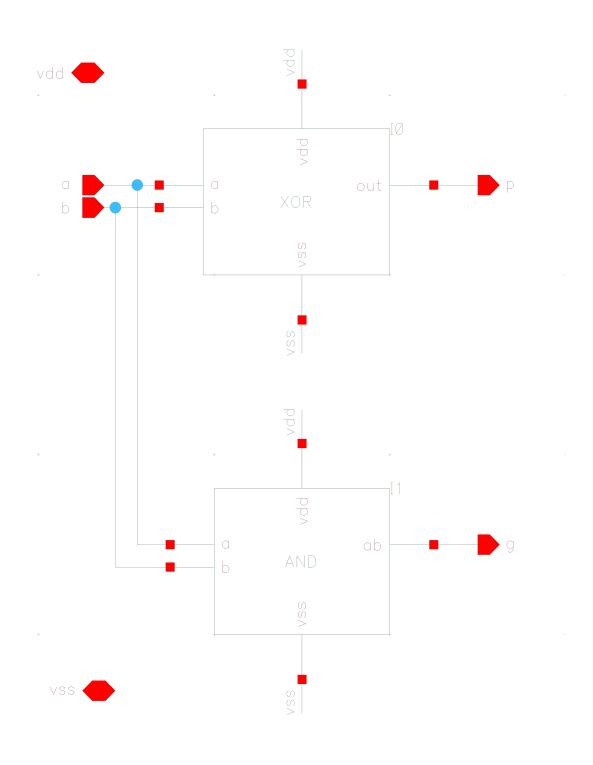


Figure 1 – Figure shows whats inside the red block in the adder


2.3 Comparator February 16, 2016

2.3 Comparator

2.3.1 Yellow

Table 2 – Logic table of yellow block.

Input	Function1	Function2	Output
00	1	0	1
01	0	0	1
10	0	0	1
11	1	0	1

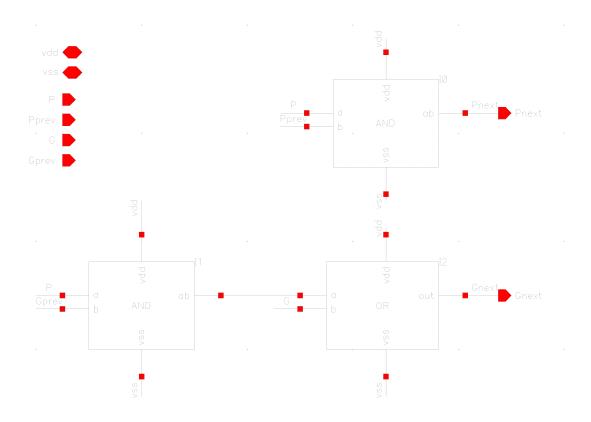

 ${\bf Figure~2}-{\rm Figure~shows~whats~inside~the~yellow~block~in~the~adder}$


2.3.2 Yellow with carry

 ${\bf Table} \ {\bf 3} - {\rm Logic} \ {\rm table} \ {\rm of} \ {\rm yellow} \ {\rm with} \ {\rm carry} \ {\rm block}.$

Input	Function1	Function2	Output
00	1	0	1
01	0	0	1
10	0	0	1
11	1	0	1

3

2.3 Comparator February 16, 2016

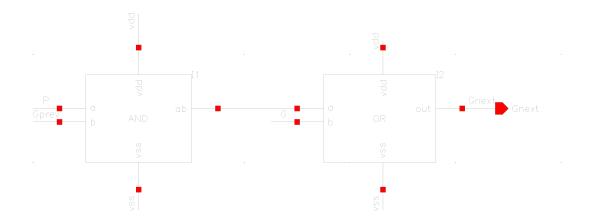

 ${\bf Figure~3}$ – Figure shows whats inside the yellow carry block in the adder

2.3.3 Sum

 ${\bf Table}~{\bf 4}-{\rm Logic~table~of~sum~block}.$

Input	Function1	Function2	Output
00	1	0	1
01	0	0	1
10	0	0	1
11	1	0	1

2.3 Comparator February 16, 2016

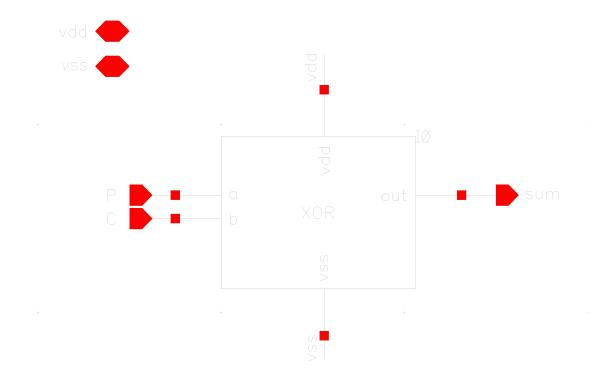


Figure 4 – Figure shows whats inside the sum block in the adder