TSEK06 High-Level Design Report

Group 5

Editor: Johannes Klasson

Version P1B

Status

Reviewed	Johannes Klasson	2016-02-15
Approved	Martin Nielsen-Lönn	-

PROJECT IDENTITY

 $\begin{tabular}{ll} VT, 2016, Group 5 \\ Linköpings Tekniska Högskola, ISY \end{tabular}$

${\bf Group\ members}$

Name	Responsibility	Phone	E-mail
Johan Isaksson	Project Leader	070-2688785	johis024@student.liu.se
Johannes Klasson	Document Manager	073-8209003	johkl226@student.liu.se
Jonas Tarasso	Designer	070-5738583	jonta760@student.liu.se
Alexander Yngve	Designer	076-2749762	aleyn573@student.liu.se

 $\mathbf{Customer} \colon \mathrm{ISY}$

Contact at customer: Martin Nielsen-Lönn Course resposible: Atila Alvandpour Consultant: Martin Nielsen-Lönn

Contents

1	Introduction	1
2	Block Level Description	1
	2.1 SPI/PSRBR	1
	2.2 16-bit Kogge-Stone Adder	1
	2.2.1 Red	1
	2.2.2 Yellow	2
	2.2.3 Yellow with carry	:
	2.2.4 Sum	;
	2.3 Comparator	4
3	Simulation Results	4
	3.1 SPI In	4
	3.1.1 Recieve	4
	3.1.2 Hanken 2	4
	3.1.3 Hanken 3	4
	3.2 Kogge-Stone Adder	4
	3.3 SPI Out	4
	3.4 Comparator	4
	3.5 Top Level	4
4	Risks and Delays	4
\mathbf{A}	Time Report	4

CONTENTS February 16, 2016

Document history

Version	Date	Changes	Performed by
P1A	2016-02-15	First draft	Johan Isaksson

1 Introduction

2 Block Level Description

2.1 SPI/PSRBR

2.2 16-bit Kogge-Stone Adder


The Kogge-Stone adder consists of four simple blocks connected in a complex way.

Lägg till bild på hur blocken sitter ihop och förklaring om P och G signalerna.

2.2.1 Red

Table 1 – Logic table of red block.

A_i	B_i	$P = A_i \oplus B_i$	$G = A_i \wedge B_i$
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

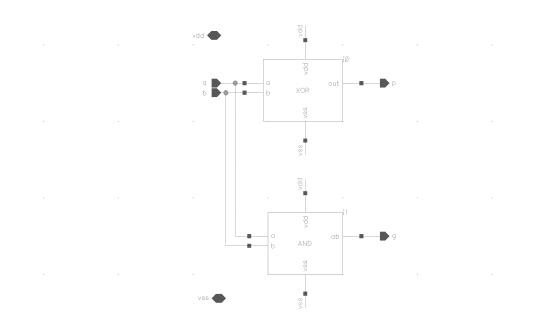

 ${\bf Figure} \ {\bf 1} - {\bf Schematic} \ {\bf view} \ {\bf of} \ {\bf the} \ {\bf red} \ {\bf block}.$

2.2.2 Yellow

Table	Z –	Logic	table	OI	yenow	DIOCK.

G_i	$G_{i,prev}$	P_i	$P_{i,prev}$	$P = P_i \wedge P_{i,prev}$	$G = (P_i \wedge G_{i,prev}) \vee G_i$
0	0	0	0	0	0
0	0	0	1	0	0
0	0	1	0	0	0
0	0	1	1	1	0
0	1	0	0	0	0
0	1	0	1	0	0
0	1	1	0	0	1
0	1	1	1	1	1
1	0	0	0	0	1
1	0	0	1	0	1
1	0	1	0	0	1
1	0	1	1	1	1
1	1	0	0	0	1
1	1	0	1	0	1
1	1	1	0	0	1
1	1	1	1	1	1


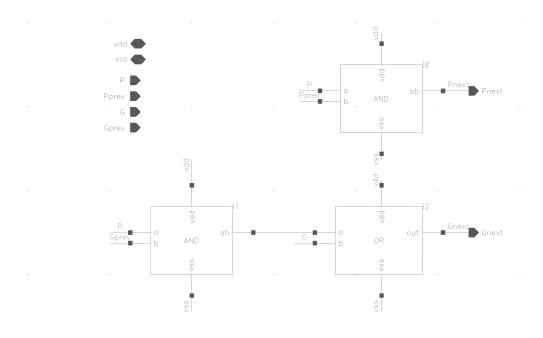


Figure 2 – Schematic view of the yellow block.

2.2.3 Yellow with carry

Table 3 – Logic table of yellow with carry block.

P_i	G_i	$G_{i,prev}$	$G = (P_i \wedge G_{i,prev}) \vee G_i$
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

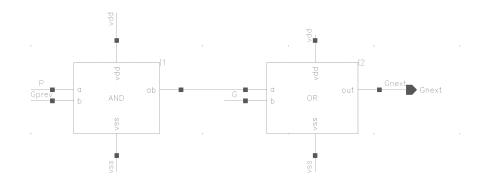

 ${\bf Figure~3}-{\bf Schematic~view~of~the~yellow~carry~block}.$

2.2.4 Sum

 ${\bf Table}~{\bf 4}-{\bf Logic~table~of~sum~block}.$

P_i	C_{i-1}	$S_i = P_i \oplus C_{i-1}$
0	0	0
0	1	1
1	0	1
1	1	0

2.3 Comparator February 16, 2016

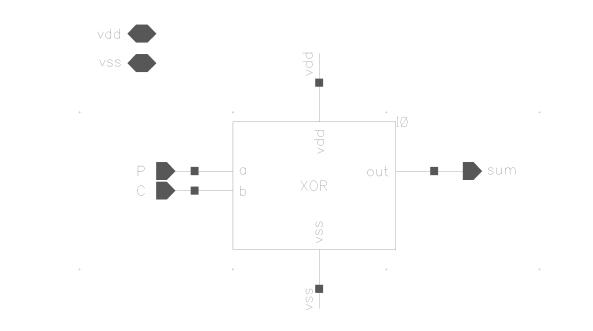


Figure 4 – Schematic view of the sum block.

2.3 Comparator

3 Simulation Results

- 3.1 SPI In
- 3.1.1 Recieve
- 3.1.2 Hanken 2
- 3.1.3 Hanken 3
- 3.2 Kogge-Stone Adder
- 3.3 SPI Out
- 3.4 Comparator
- 3.5 Top Level

4 Risks and Delays

A Time Report